

**ECE272 Lab 4**  
**Spring 2018**

**Driving multi-digit LED displays**  
**Isak Foshay**

**May 13<sup>th</sup>, 2018**

## 1. Introduction

This lab aims to teach students about system verilog and all of it's charm. It aims to teach students the concept of digital wires and the transfer of data through software via digital wires. This lab also teaches about state machines (However simple the state machine used is it is still a state machine). The lab also touches on persistence of vision.

## 2. Design

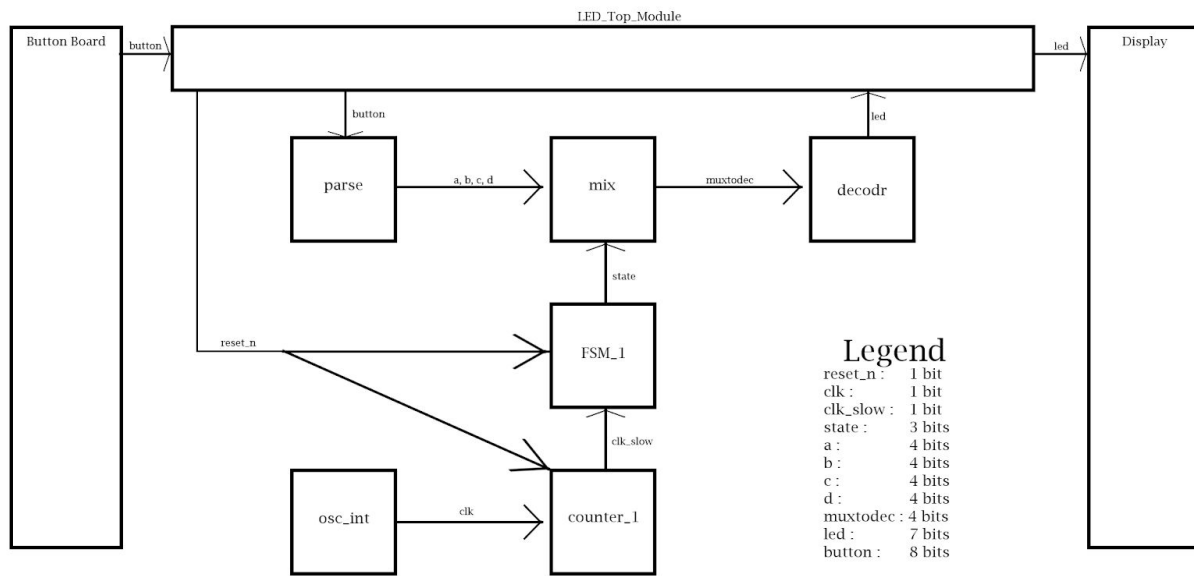


Figure 1: Design of how software works

This project took a long time so some of the names are 5th or 6th attempts at making it work so the names had devolved into semi-obscurity. Particularly mux turned into mix and decoder turned into decodr. They still get their point across and they work so I kept it as is as a tribute to the modules that finally worked. Reset comes from the top module so I had to get creative with the arrows for reset\_n. I feel this accurately portrays the flow of how the software works.

|           | FPGA PIN | PULLMODE |
|-----------|----------|----------|
| button[0] | F5       | UP       |
| button[1] | E3       | UP       |
| button[2] | B1       | UP       |
| button[3] | C1       | UP       |
| button[4] | D2       | UP       |
| button[5] | E2       | UP       |
| button[6] | F2       | UP       |
| button[7] | G1       | UP       |
| reset_n   | C2       | UP       |
| led[0]    | G14      | DOWN     |
| led[1]    | B16      | DOWN     |
| led[2]    | D14      | DOWN     |
| led[3]    | F14      | DOWN     |
| led[4]    | D16      | DOWN     |
| led[5]    | C15      | DOWN     |
| led[6]    | E16      | DOWN     |
| state[0]  | E7       | DOWN     |
| state[1]  | E8       | DOWN     |
| state[2]  | F9       | DOWN     |

Table 1: Chosen Pins and Pull Modes

I tried to group my pins together in an at least semi consistent manner. I also made sure to assign reset\_n to a pin far from my other pins I was actively using and plugging things into.

 


Figure 2a: Block Diagram for Hardware

This diagram shows that we are using all 8 buttons on our button board, and also shows which pin to connect each button to.

 


Figure 2b: Block Diagram for Hardware

This diagram shows that the state selection is no longer up to the user like lab 3 and is instead handled by the FPGA itself. It also informs whoever is setting up the wires what needs to be plugged into what.

### **3. Results**

My result was a working seven segment display that could display on each digit and did not appear to flicker.

### **4. Experiment Notes**

I attended 5 labs in order to finish this, as well as many many hours outside of lab. I partly blame this lab for my end of term weight gain because of how much this project stressed me out. There was little to no system verilog documentation available anywhere and it took me hours to figure out how things worked. This lab was the most difficult and stressful lab I have ever taken. But at the same time I learned the most from this lab. However, there are definitely less painful and time consuming ways to learn system verilog.

#### **Study Questions:**

##### **1. Describe the differences between Mealy and Moore state machines..**

Mealy does an action when you land on the state, Moore you do an action when moving to a new state.

## Appendix

Code:

---

```
module clock_counter(
    input logic clk_i,           //often, "tags" are added to variables to denote what they do for the user
    input logic reset_n,         //here, 'i' is used for input and 'o' for the output, while 'n' specifies
                                //an active low signal ("not")
    output logic clk_o
);

    logic [13:0] count;          //register stores the counter value so that it can be modified
                                //on a clock edge. Register size needs to store as large of a
                                //number as the counter reaches. Here,  $2^{(13+1)} = 16,384$ .

    always_ff @(posedge clk_i, negedge reset_n)
    begin
        count <= count + 1;      //at every positive edge, the counter is increased by 1
        if(!reset_n) //If reset_n gets pulled to ground (active low), reset count to 0
        begin
            clk_o <= 0;
            count <= 0;
        end
    else
        if(count >= 5000) //Flips the slow clock every 10000 clock cycles
        begin
            clk_o <= ~clk_o;      //Flip slow clock
            count <= 0;           //Reset the counter
        end
    end
endmodule
```

---

```
module LED_top_module(
    /******
    /* Set inputs and outputs */
    /* to the whole FPGA here */
    /******
    input logic reset_n, //be sure to set this input to PullUp, or connect the pin to 3.3V
    input logic [7:0] button,
    output logic [2:0] state,
    output logic [6:0] led
);
    /******
    /* Set internal variables here */
    /******
    logic clk;           //used for the oscillator's 2.08 MHz clock
    logic clk_slow;       //used for slowed down, 5 Hz clock
    logic [3:0] a;
    logic [3:0] b;
    logic [3:0] c;
    logic [3:0] d;
    logic [3:0] muxtodec;
    /******
    /* Define modules here */
    /******
    parser parse (
        .inp(button),
        .a(a),
        .b(b),
```

```

.c(c),
.d(d)
);

mux2 mix (
.a(a),
.b(b),
.c(c),
.d(d),
.s(state),
.y(muxtodec));

sevenseg decodr (
.data(muxtodec),
.segments(led)
);

//This is an instance of a special, built in module that accesses our chip's oscillator
OSCH #("2.08") osc_int ( // "2.08" specifies the operating frequency, 2.08 MHz.
//Other clock frequencies can be found in the
MachX02's documentation
.STDBY(1'b0), //Specifies active state
.OSC(clk), //Outputs clock signal to 'clk' net
.SEDSTDBY()); //Leaves SEDSTDBY pin unconnected

//This module is instantiated from another file, 'Clock_Counter.sv'
//It will take an input clock, slow it down based on parameters set inside of the module, and
//output the new clock. Reset functionality is also built-in
clock_counter counter_1(
.clk_i(clk),
.reset_n(reset_n),
.clk_o(clk_slow));

//This module is instantiated from another file, 'State_Machine.sv'
//It contains a Moore state machine that will take a clock and reset, and output a state
state_machine FSM_1(
.clk_i(clk_slow),
.reset_n(reset_n),
.state(state)
);

/*****
/* Add modules for: */
/* Parser Determines the 1000's, 100's, 10's and 1's place of the number*/
/* Multiplexer Determines which parser output to pass to the decoder */
/* Decoder Convert 4-bit binary to 7-seg output for numbers 0-9 */
*****/

endmodule

```

---

```

module state_machine( //example of a Moore type state machine
input logic clk_i,
input logic reset_n,

output logic [2:0] state //The state outputted by this state machine
);

//next state register

```

```

logic [2:0] state_n;

//each possible value of the state register is given a unique name for easier use later
parameter S0 = 3'b000; //First digit
parameter S1 = 3'b001; //Second digit
parameter S2 = 3'b011; //Third digit
parameter S3 = 3'b100; //Fourth digit

//asynchronous reset will set the state to the start, S0, otherwise, the state is changed
//on the positive edge of the clock signal
always_ff @(posedge clk_i, negedge reset_n)
begin
    if(!reset_n)
        state = S0;
    else
        state = state_n;

end

//this section defines what the next state should be for each possible state. in this
//implementation, it simply rotates through each state automatically
always_ff @(*)
begin
    case(state)
        S0: state_n = S1;
        S1: state_n = S2;
        S2: state_n = S3;
        S3: state_n = S0;

        default: state_n = S0;

    endcase
end
endmodule

```

---

```

module sevenseg(
    input logic [3:0] data,
    output logic [6:0] segments );
always @(*)
    case( data ) // 7'bABCDEFGH
        0: segments = 7'b1000000;
        1: segments = 7'b1111001;
        2: segments = 7'b0100100;
        3: segments = 7'b0110000;
        4: segments = 7'b0011001;
        5: segments = 7'b0010010;
        6: segments = 7'b0000010;
        7: segments = 7'b1111000;
        8: segments = 7'b0000000;
        9: segments = 7'b0011000;
        default: segments = 7'b1111111;
    endcase
endmodule

```

---

```

module mux2 ( input [3:0] a,
               input [3:0] b,
               input [3:0] c,
               input [3:0] d,
               input [2:0] s,
               output logic [3:0] y);

```



```
always @ (a or b or c or d or s)
case (s)
  3'b100 : y = a;
  3'b011 : y = b;
  3'b001 : y = c;
  3'b000 : y = d;
  default: y = a;
endcase
endmodule
```

---

```
module parser (
  input logic [7:0] inp,
  output logic [3:0] a,
  output logic [3:0] b,
  output logic [3:0] c,
  output logic [3:0] d);

  //assign a = (inp - (inp%1000))/1000;
  //assign b = ((inp%1000)-(inp%100))/100;
  //assign c = ((inp%100)-(inp%10))/10;
  //assign d = (inp%10);
  assign a = (inp/1000)%10;
  assign b = (inp/100)%10;
  assign c = (inp/10)%10;
  assign d = (inp % 10);
endmodule
```